



Noise Considerations in Microwave Operational Transconductance Amplifiers (OTAs)



Carlos Saavedra
Professor, Queen's University, Canada

Acknowledgments



- Current and former graduate students:
 - You Zheng
 - Jiangtao Xu
 - Fan Jiang
- Funding support:
 - Natural Sciences and Engineering Research Council of Canada (NSERC)
 - CMC Microsystems



Outline



- Fundamentals: OTAs and their (mostly) baseband applications
- OTAs in Microwave Circuits and Systems
- Microwave OTA circuit design
- Conclusion



Fundamentals

The basic definition of an OTA



- voltage-in / current-out amplifiers

$$i_{out+} - i_{out-} = g_m(v_{in+} - v_{in-})$$

$$g_m = f(I_{tune}, V_{DD})$$



learn to
exploit this!

- infinite input resistance
- infinite output admittance



OTA configurations





Single-ended

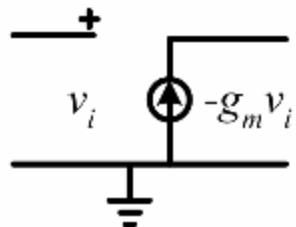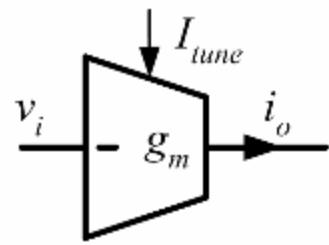



Differential input

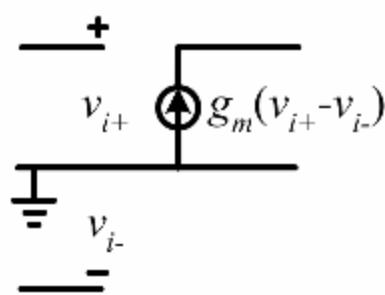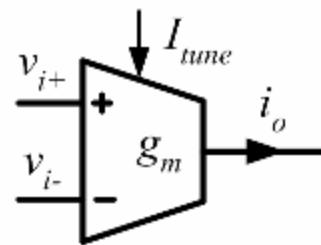

Differential input & output

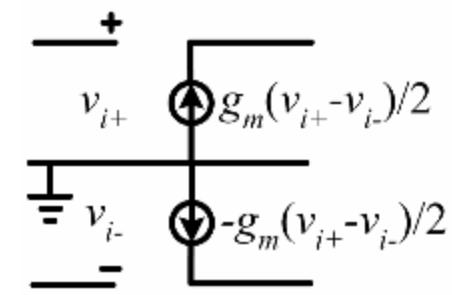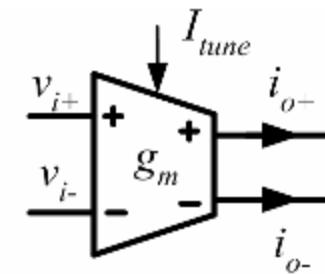


Basic OTA applications

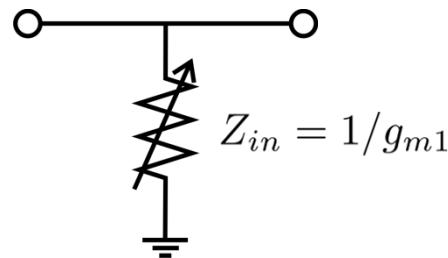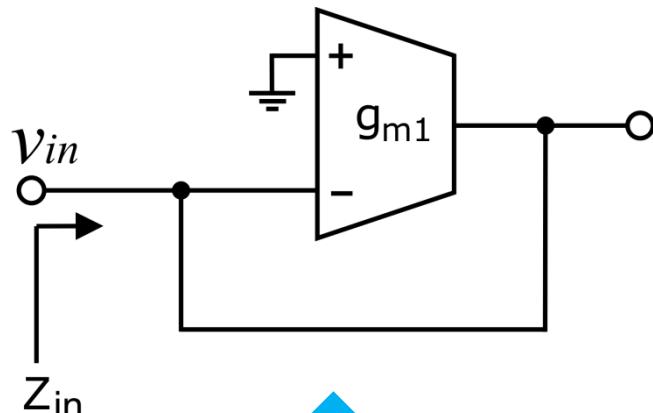

variable resistor

using the simplest
possible model.....

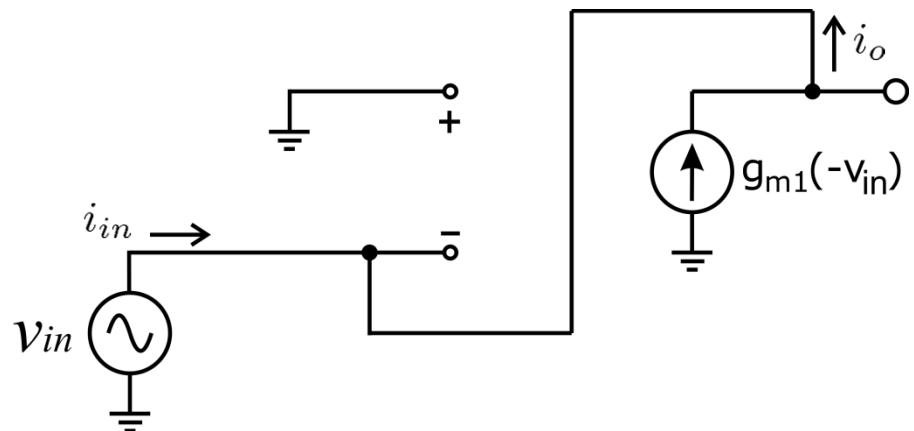

$$i_{in} = -i_o$$


$$Z_{in} = v_{in}/i_{in}$$

$$= v_{in}/(-i_o)$$



$$= v_{in}/(-(-g_{m1}v_{in}))$$

$$= 1/g_{m1}$$



Basic OTA applications

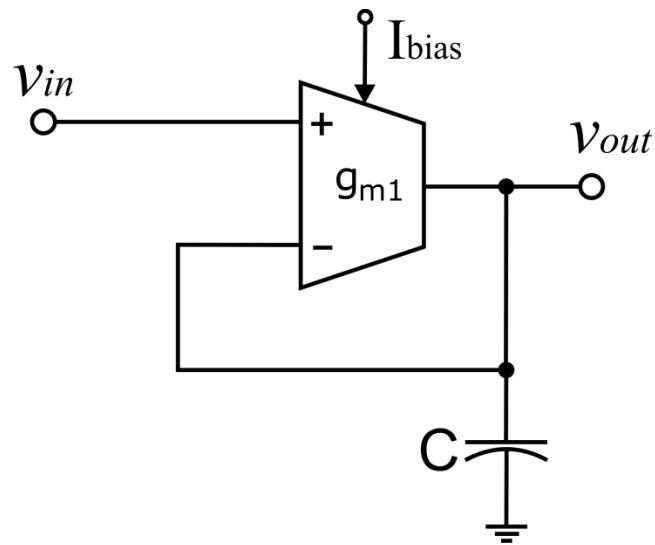

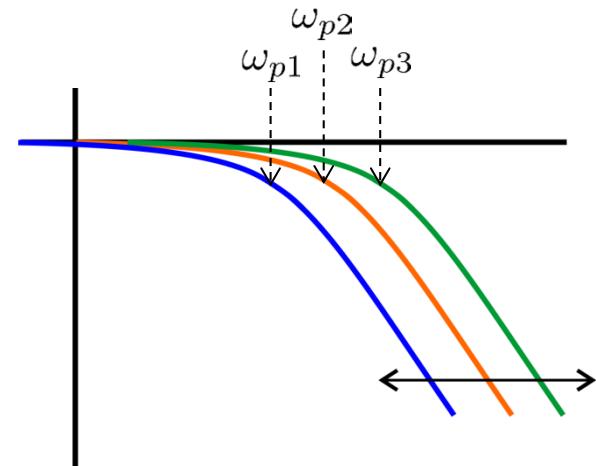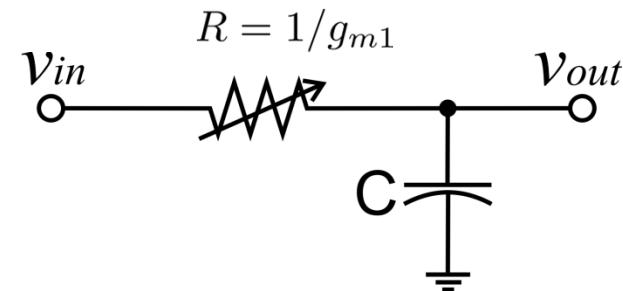
$$\begin{aligned}
 H(s) &= \frac{v_{out}(s)}{v_{in}(s)} = \frac{g_{m1}}{g_{m1} + sC} \\
 &= \frac{1}{1 + sRC} \\
 \omega_p &= \frac{g_{m1}}{C}
 \end{aligned}$$




Basic OTA applications

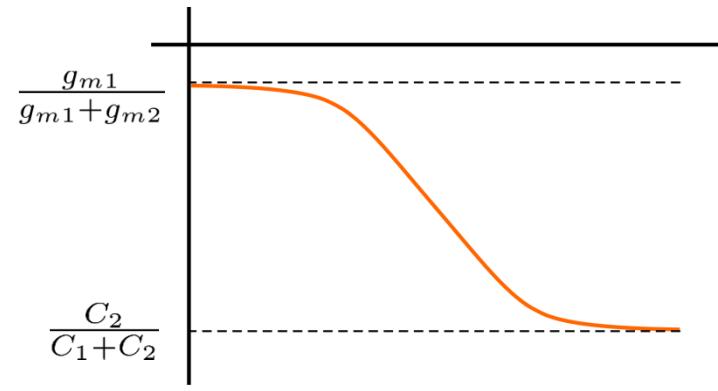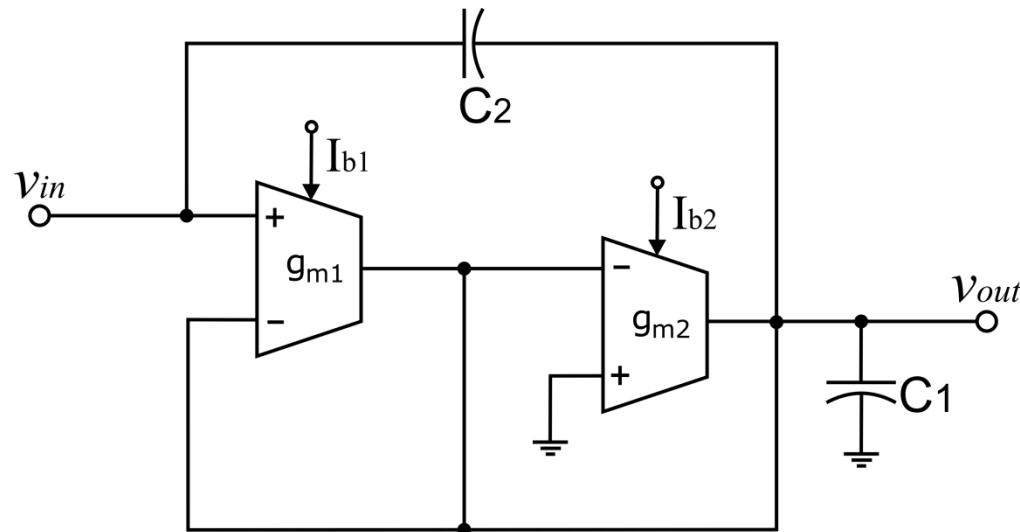
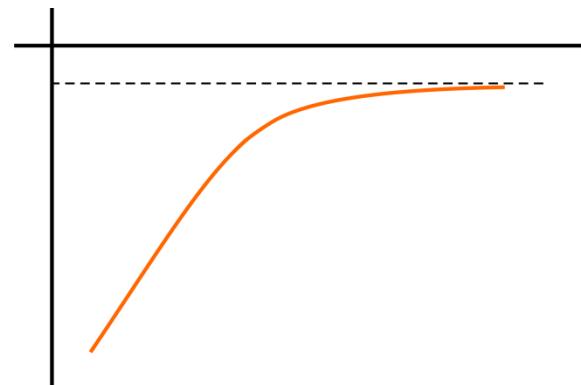
$$\frac{v_{out}}{v_{in}} = \frac{g_{m1} + sC_2}{s(C_1 + C_2) + g_{m1} + g_{m2}}$$



Basic OTA applications

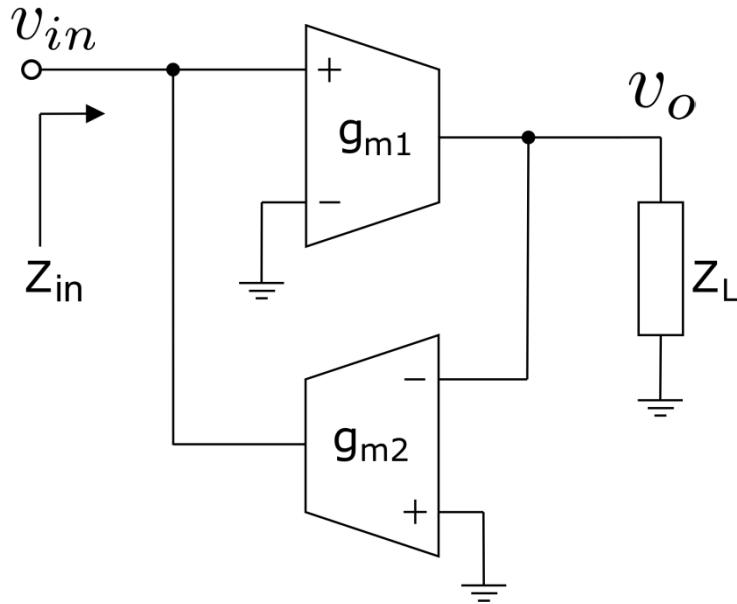

Impedance inverter

At the output,

$$v_o = g_{m1} v_{in} Z_L \quad (1)$$

and through the feedback path,

$$v_{in} = g_{m2} v_o Z_{in}$$

↳ $v_o = v_{in} / (g_{m2} Z_{in}) \quad (2)$

making eqn. (1) = eqn. (2),

$$g_{m1} v_{in} Z_L = v_{in} / (g_{m2} Z_{in}) \quad (3)$$


and solving (3) for Z_{in} yields

$$Z_{in} = 1 / (Z_L g_{m1} g_{m2}) \quad (4)$$

Basic OTA applications



$$Z_{in} = 1/(Z_L g_{m1} g_{m2})$$

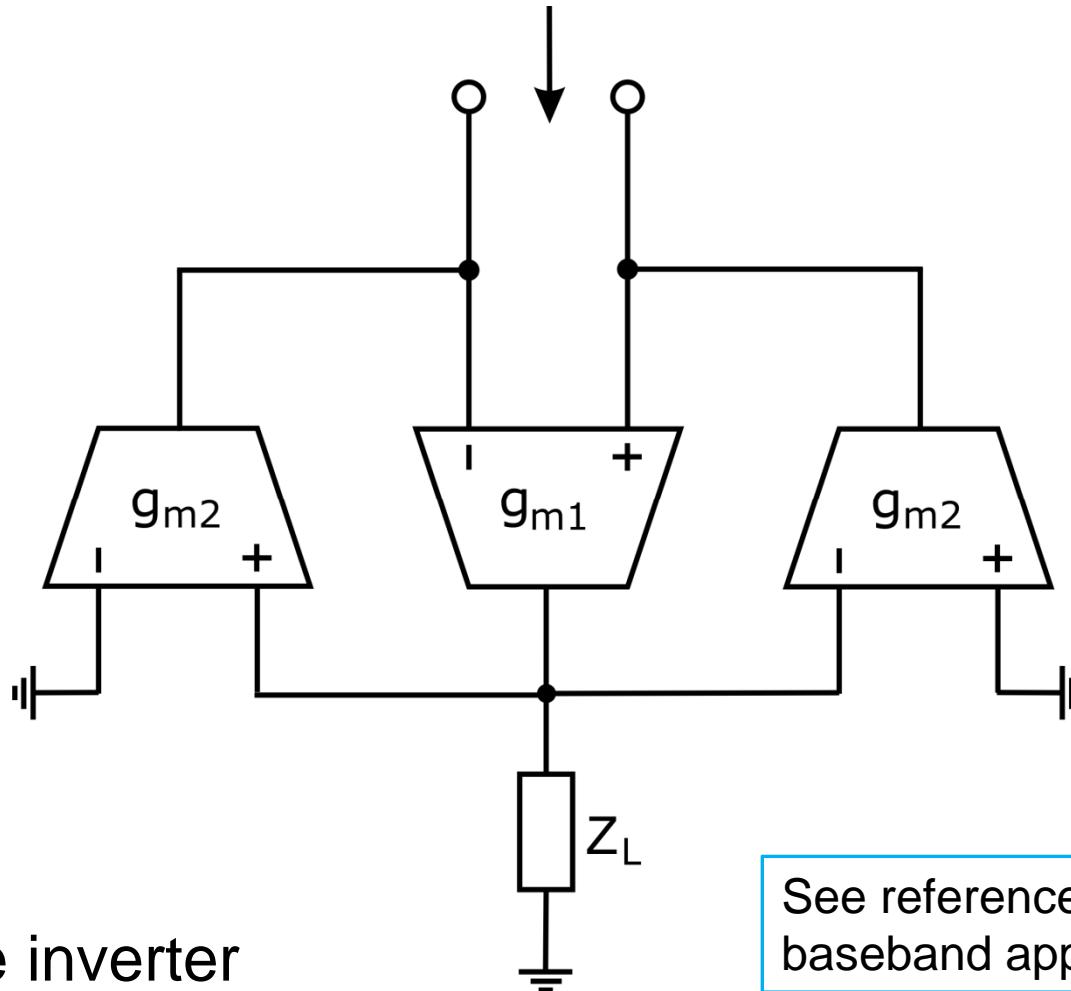


Differential
impedance inverter


See reference [1] for more
baseband applications of OTAs.





OTAs in Microwave Circuits and Systems

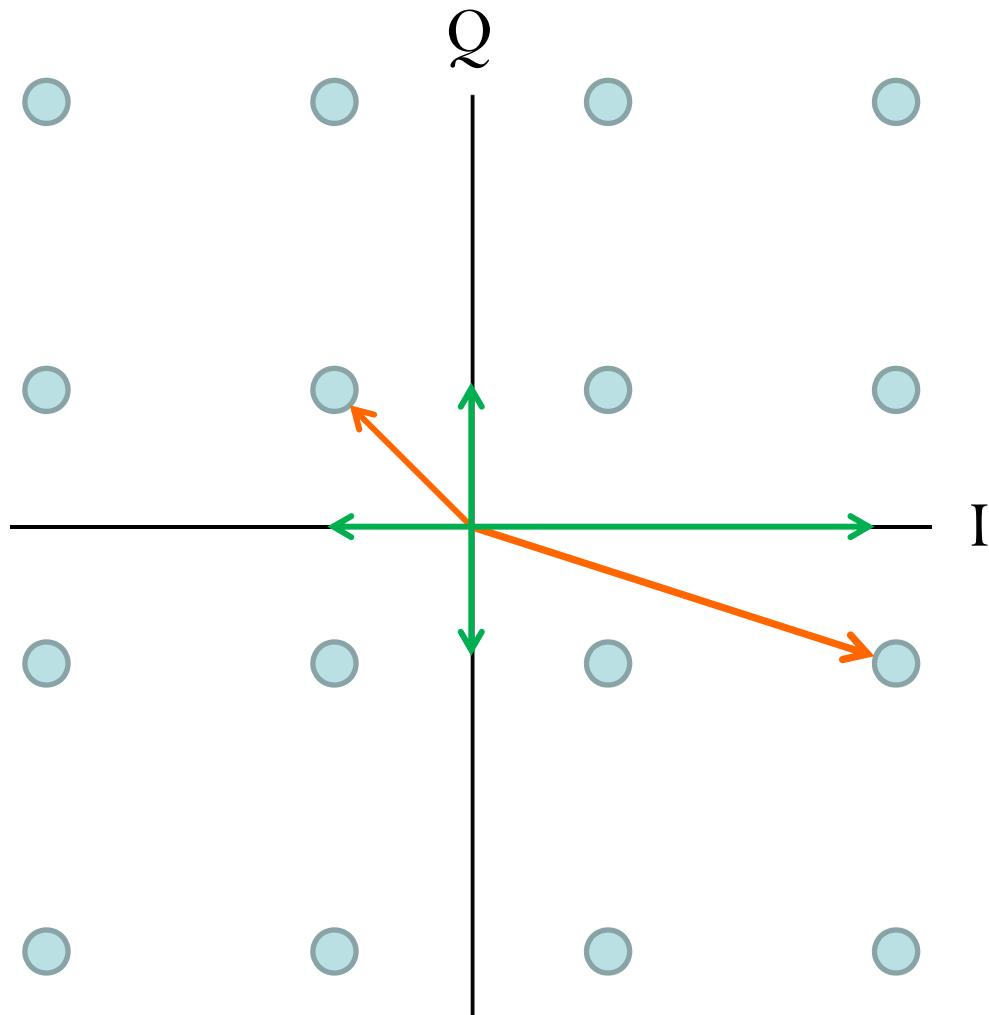

Multi-order QAM circuit

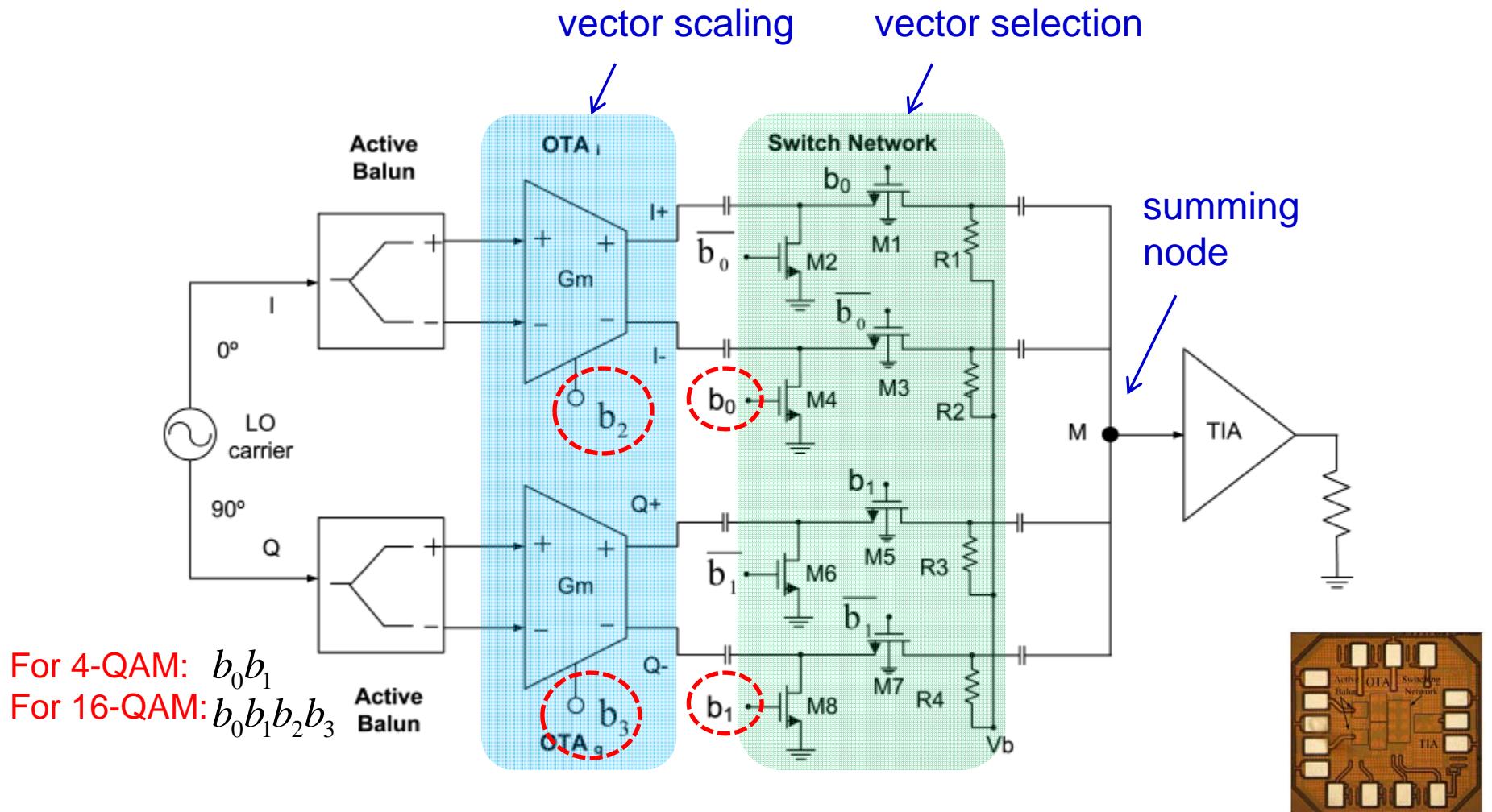



Multi-order QAM circuit

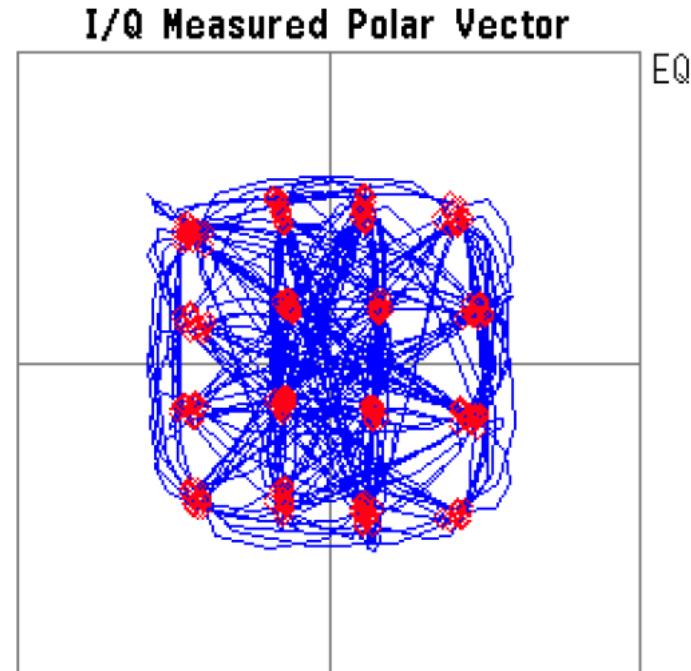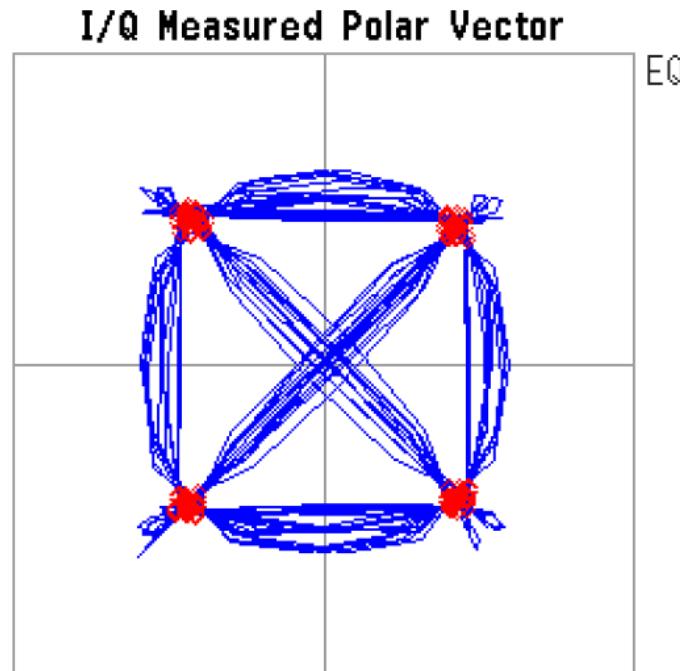

Modulation Scheme	EVM (%)	Mag Error (%)	Phase Error degree	Freq Error (Hz)	DC offset (dB)	SNR (dB)	Output Power (dBm) @ $P_{in} = -19\text{dBm}$
QPSK	2.33	1.43	1.12	-12.59	-22.13	32.14	-27.99
16-QAM	6.20	4.40	4.05	-139.96	-26.16	21.23	-21.59



For further details see [2].

Active quasi-circulator

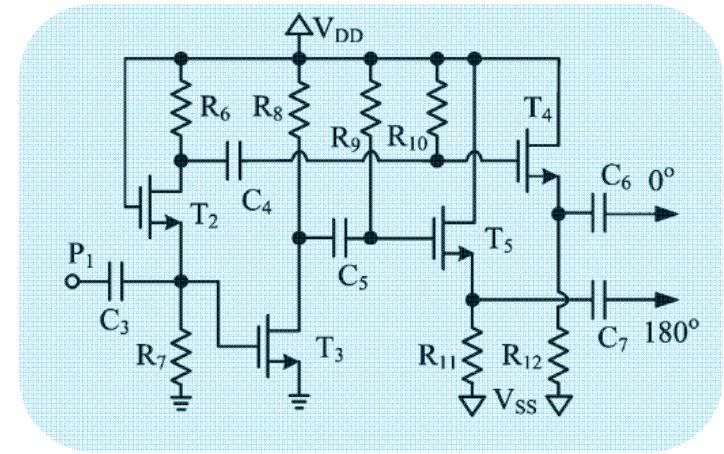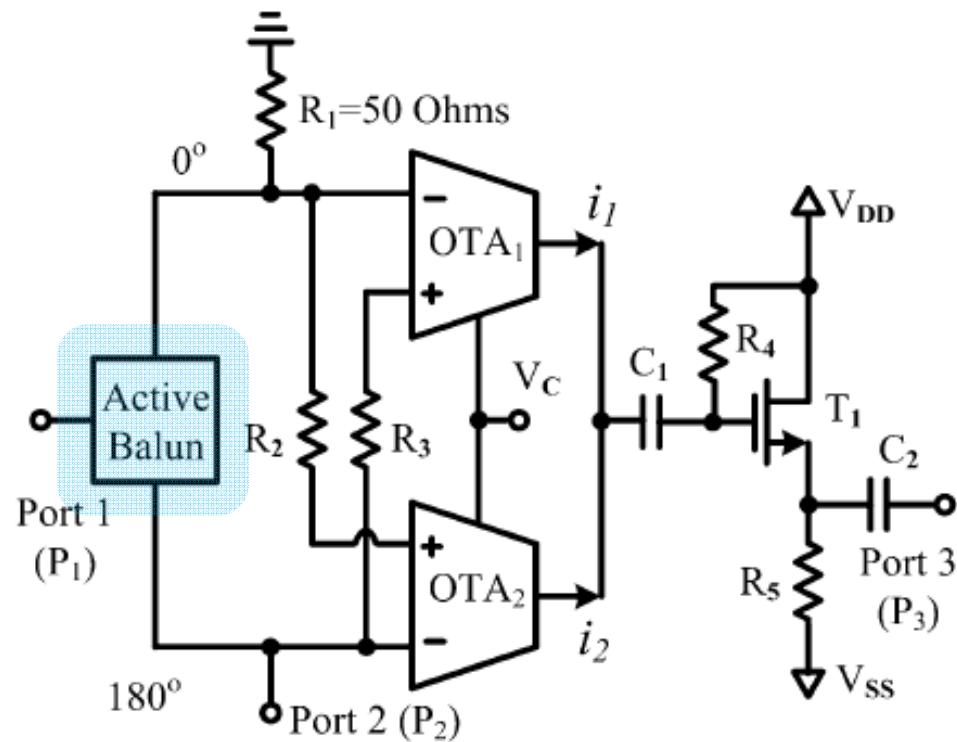

active balun


Active quasi-circulator

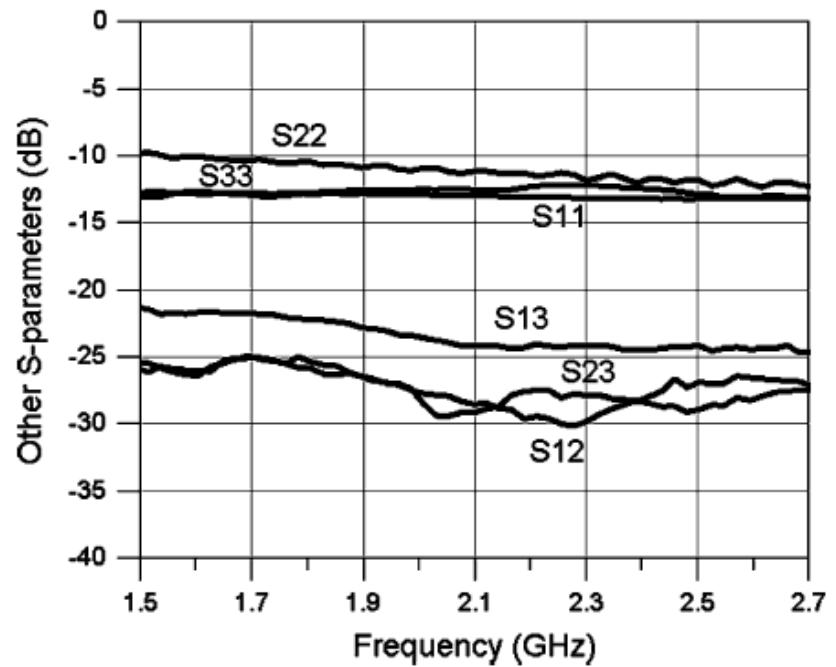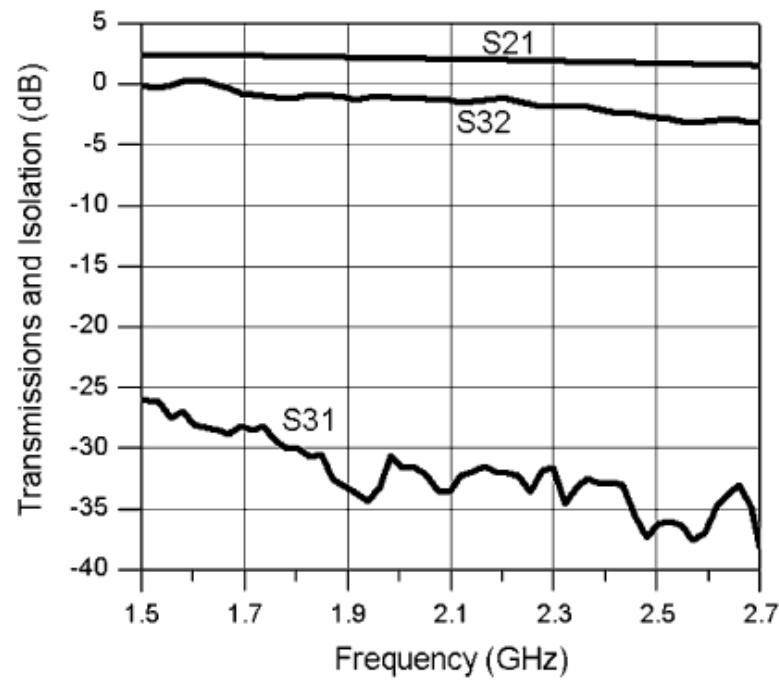

Active Quasi-Circulator




Parameter	Value
IP _{1dB}	-6.4 dBm
IIP ₃	+1.2 dBm
NF	10.4±0.2 dB
DC power	86 mW
Core size	0.25 sq. mm.
Technology	180 nm CMOS

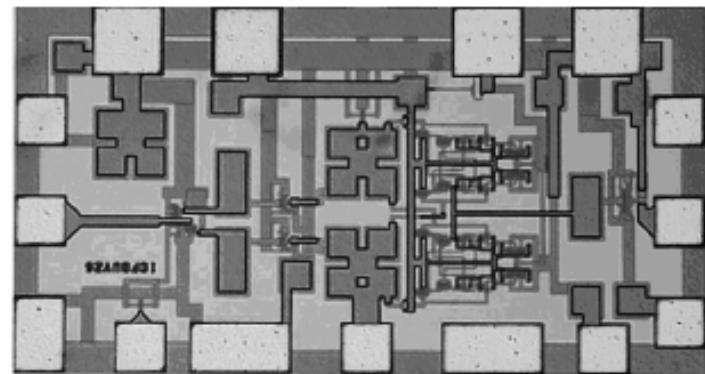

For further details see [3].

OTAs in active mixers


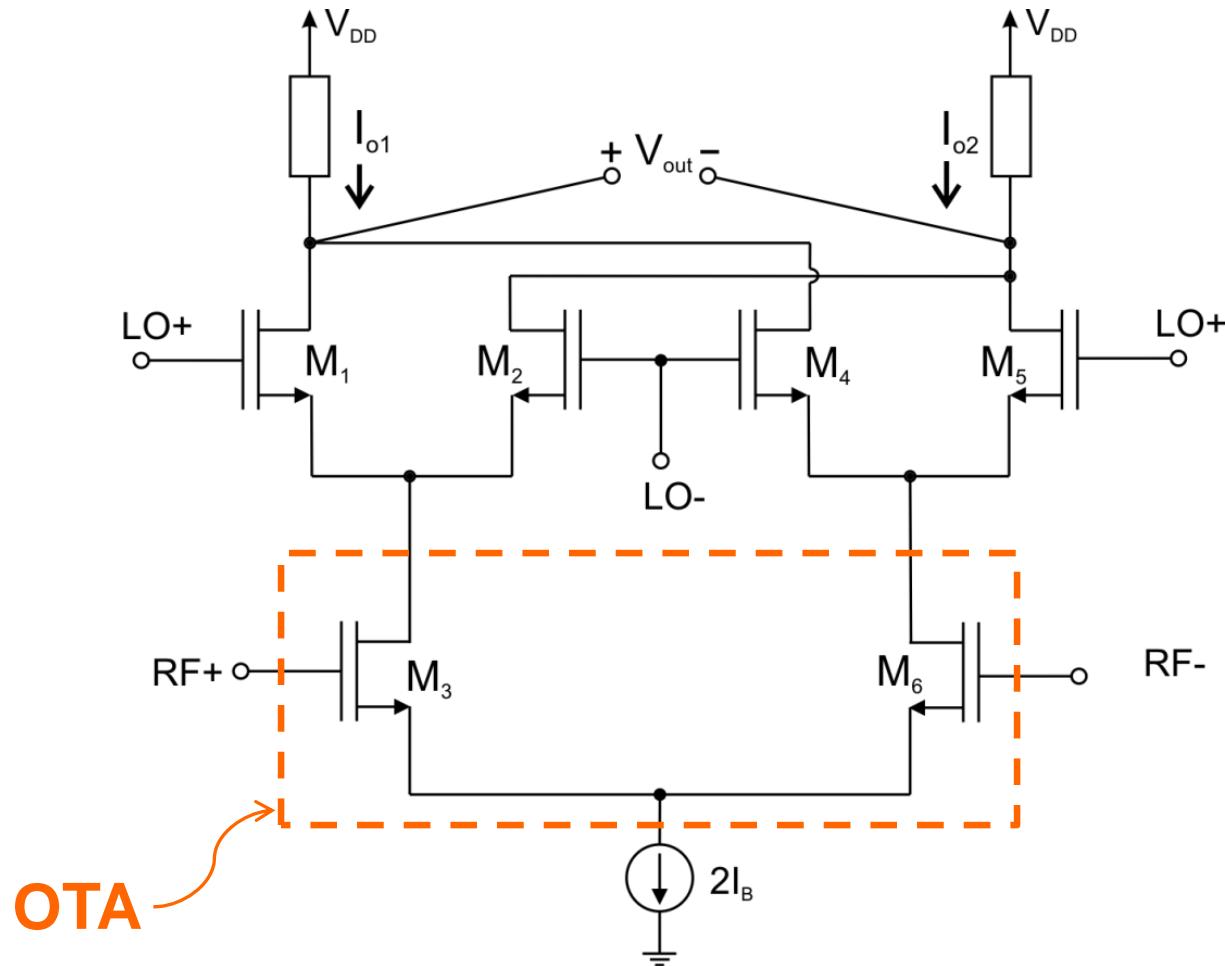






Variable conversion gain mixer

$$CG = \kappa G_m Z_L$$
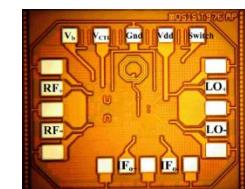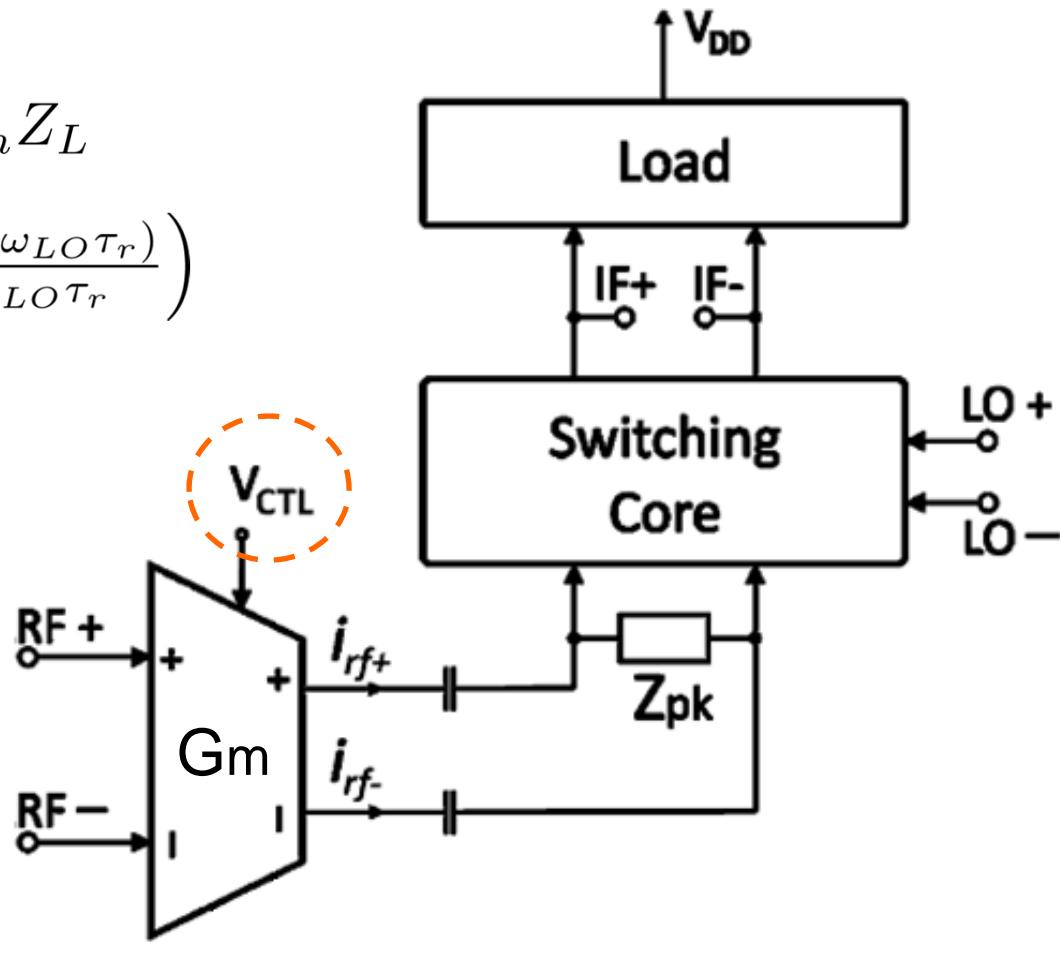
$$\kappa = \frac{2}{\pi} \left(\frac{\sin(\omega_{LO}\tau_r)}{\omega_{LO}\tau_r} \right)$$



VCG mixer

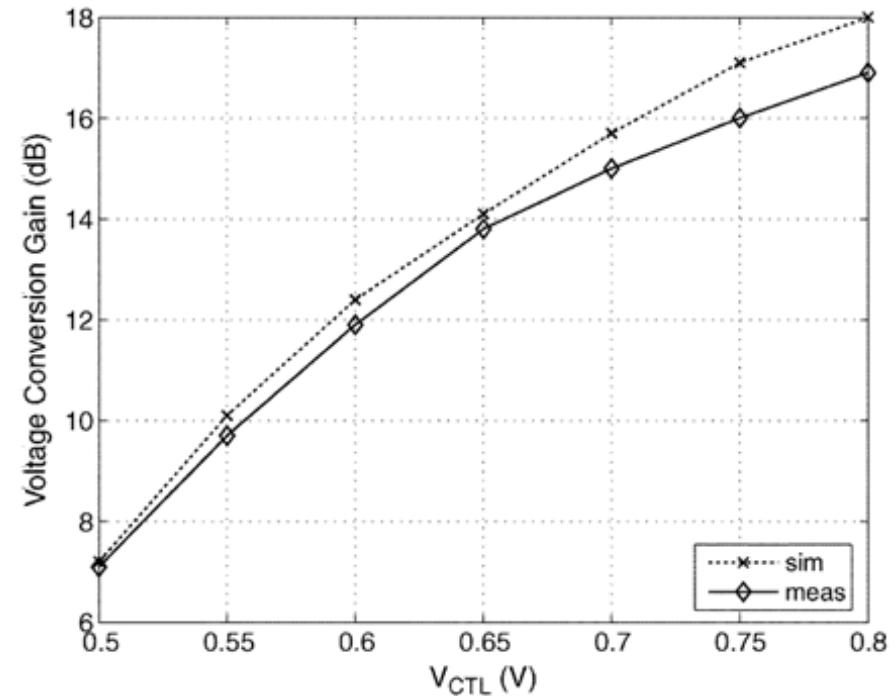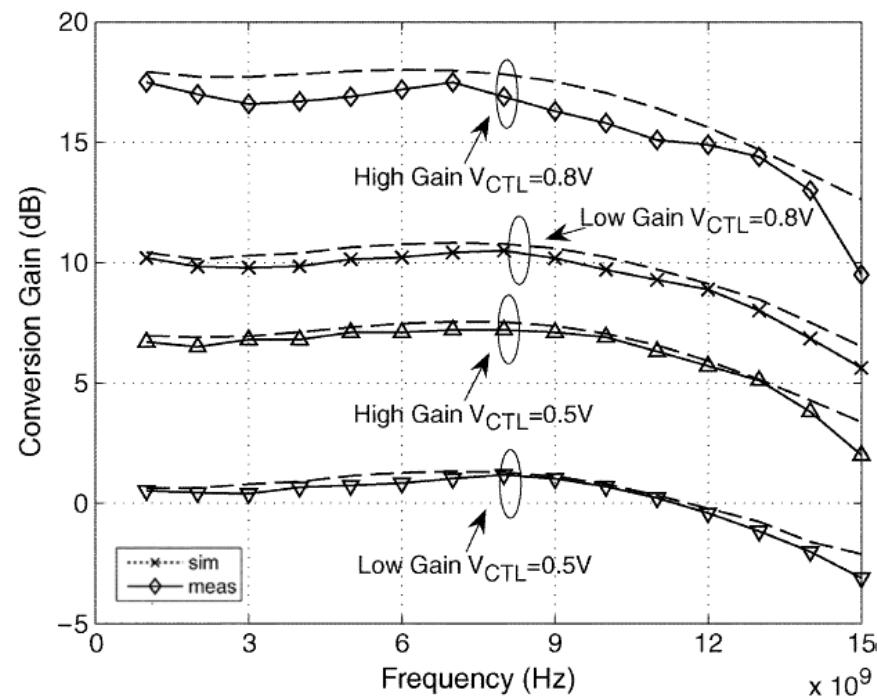

For further details see [4].

VCG mixer





Parameter	Value
RF frequency input	(GHz) 1 to 12 GHz
Conversion gain	(dB) +1.2 to +17 dB
Input P _{1dB}	(dBm) -3.7 (max) -12 (min)
Input IP3	(dBm) +8.6 (max) +2.5 (min)
DSB noise figure	(dB) 11 (min) >19 (max)
DC power	(mW) 1.8 (min) 5.9 (max)
V _{dd}	(V) 1.2
Chip core area	(sq. mm.) 0.105
CMOS node	(nm) 130




Microwave OTA Circuit Design

Full CMOS version

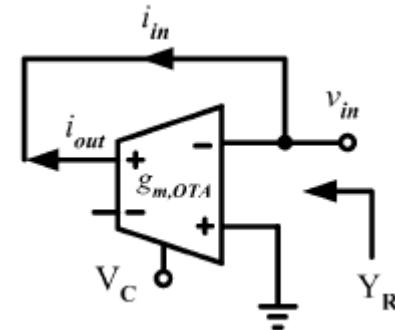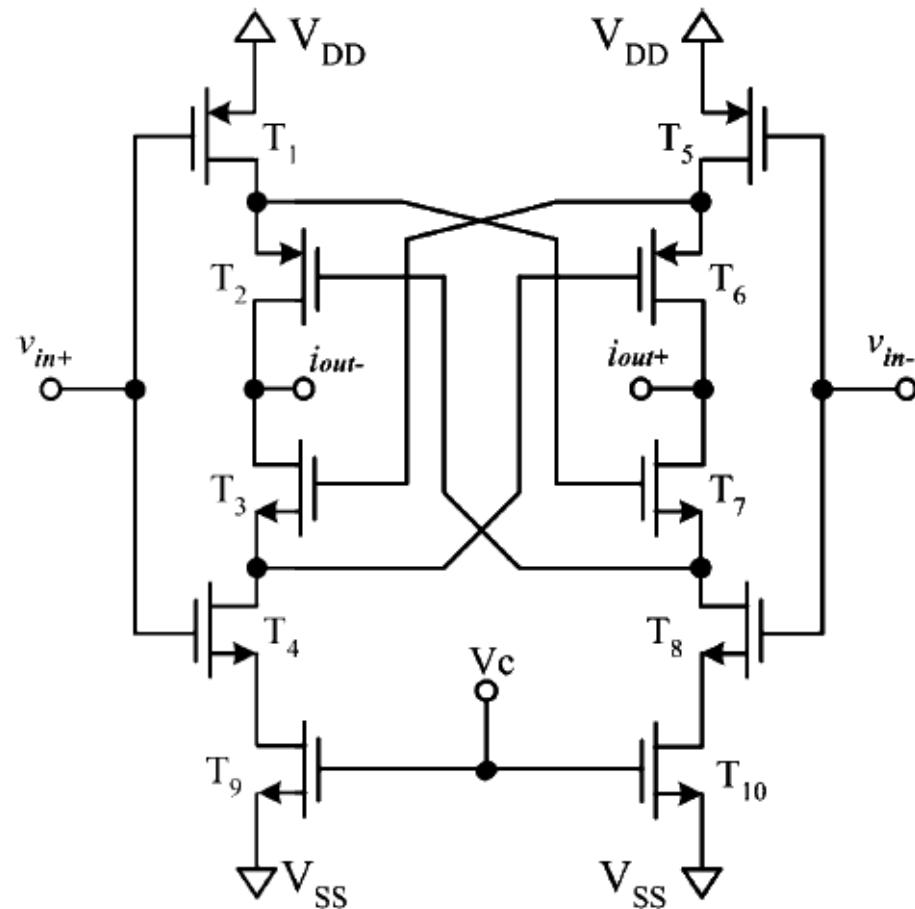


$$Y_R = Y_0 \left(\frac{1 - S_{11}}{1 + S_{11}} \right)$$

$$|g_{m,OTA}| \approx \text{Re}(Y_R)$$

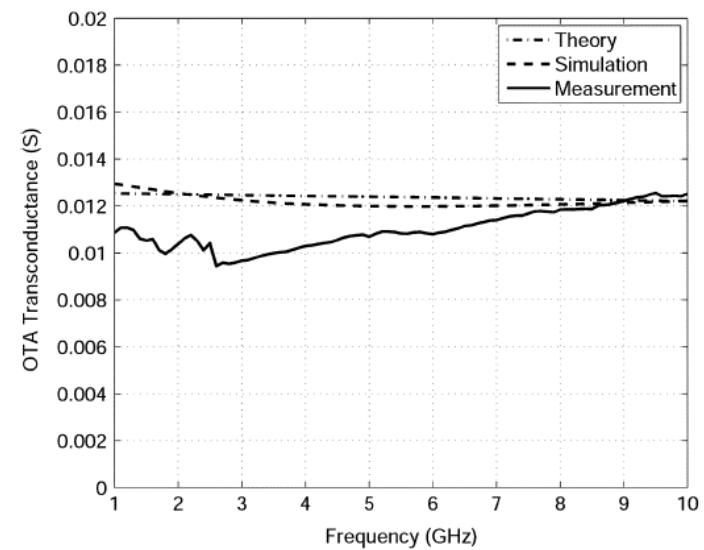

For further details see [5].

The feedforward regulated cascode OTA

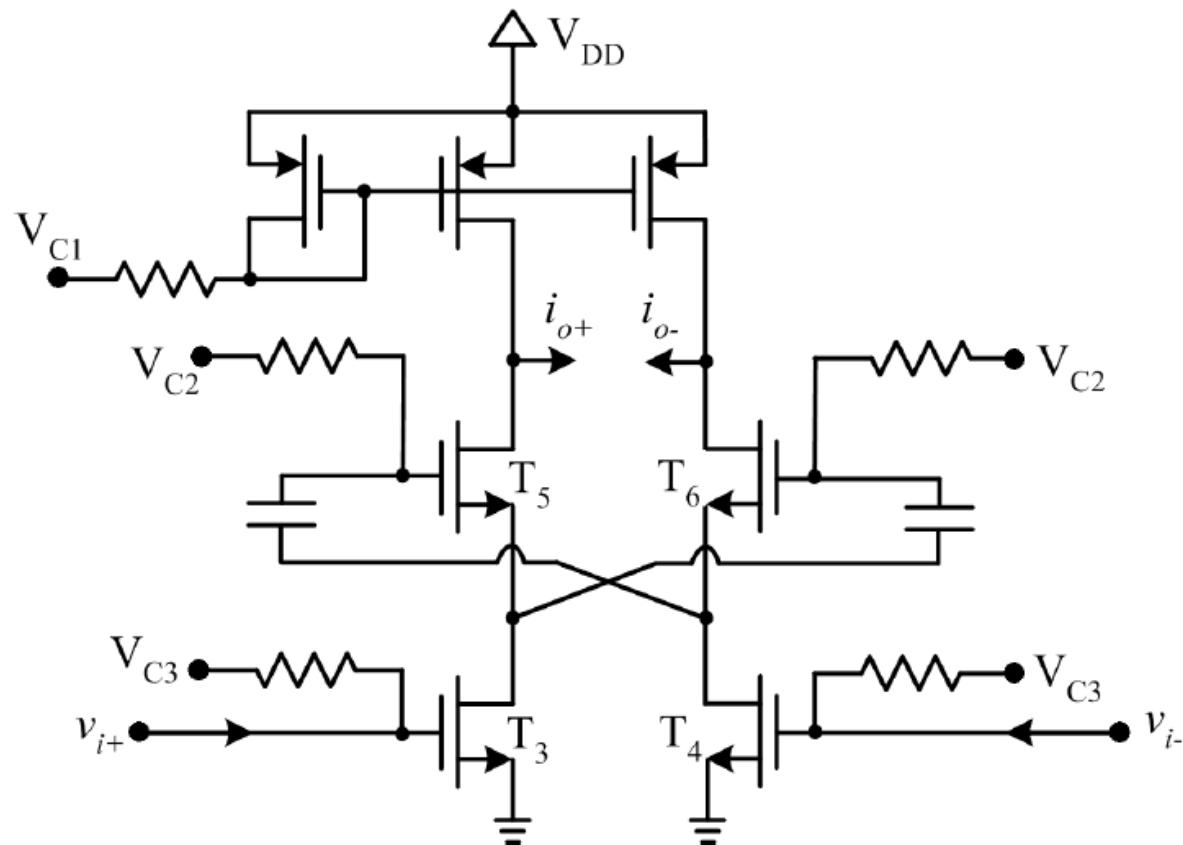

In the ideal case of a perfectly balanced circuit:

$$G_m = \frac{i_{o+} - i_{o-}}{v_{i+} - v_{i-}}$$


$$= g_{m3} \left[\frac{\frac{1}{r_{o5}} + 2g_{m5}}{\frac{1}{r_{o3}} + \frac{1}{r_{o5}} + 2g_{m5}} \right]$$

$$R_o = 2r_{o3} + 2r_{o5} + 4g_{m5}r_{o3}r_{o5}$$

For further details see [6-8].





Frequency response

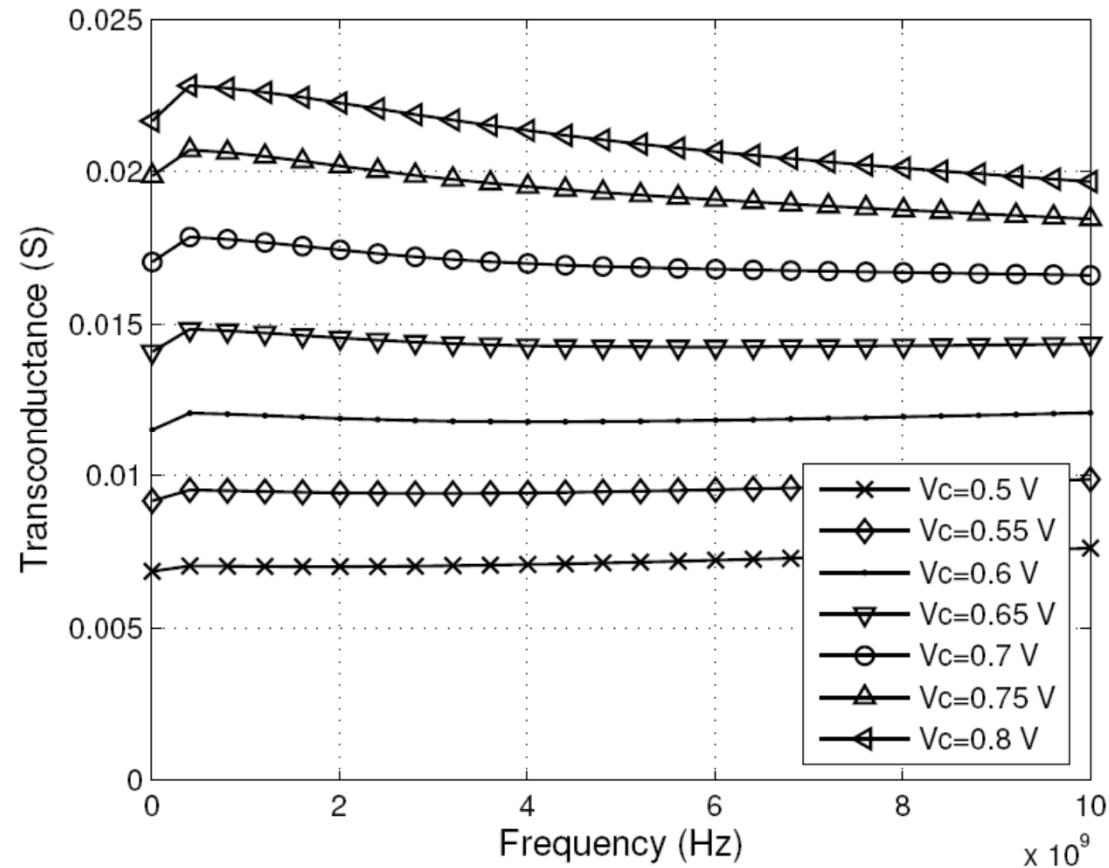

How to make a low-noise OTA?



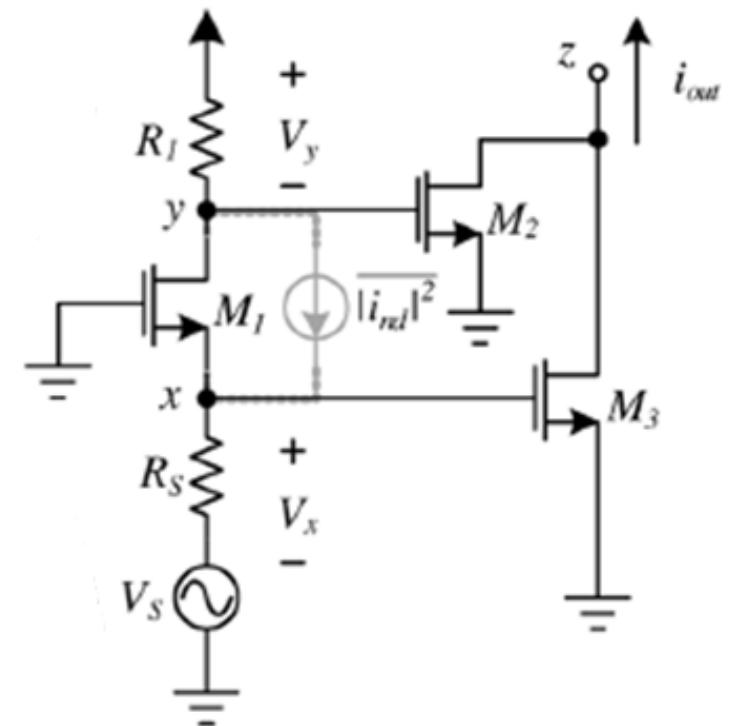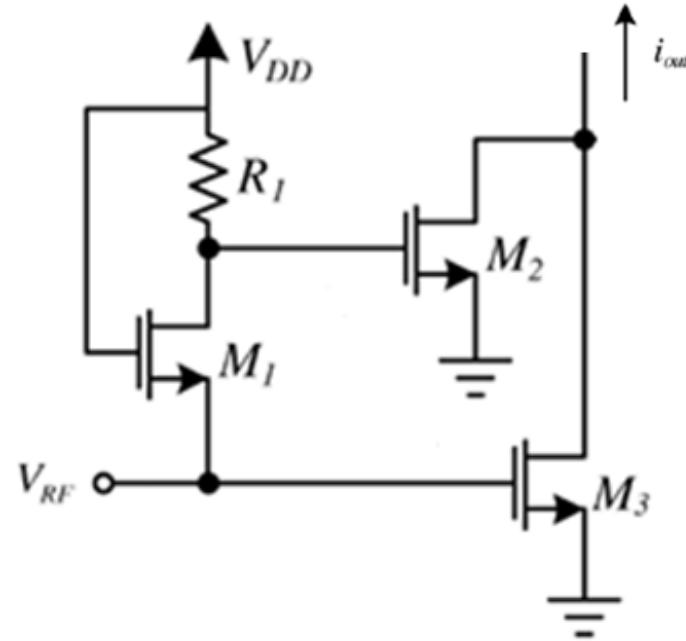
Start with the noise-cancelling method [9] used in LNAs:



Low-noise OTA (LNTA)



Cross-couple the basic cells to get:

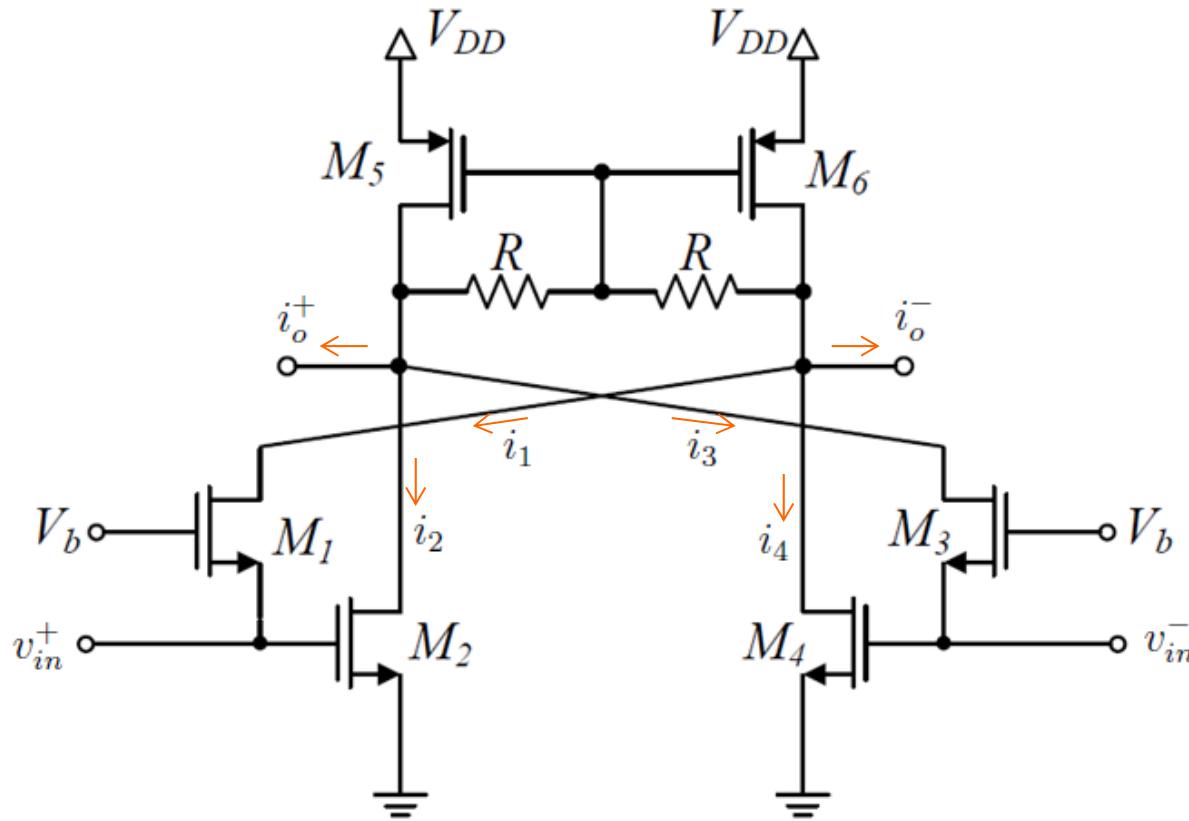


$$i_o^+ = i_2 + i_3 = g_{m2}v_{in}^+ - g_{m3}v_{in}^-$$

$$i_o^- = i_1 + i_4 = -g_{m1}v_{in}^+ + g_{m4}v_{in}^-$$

$$G_m = \frac{i_o^+ - i_o^-}{v_{in}^+ - v_{in}^-} = g_{m,CG} + g_{m,CS}$$

For further details see [10,11].

The CG-CS pair

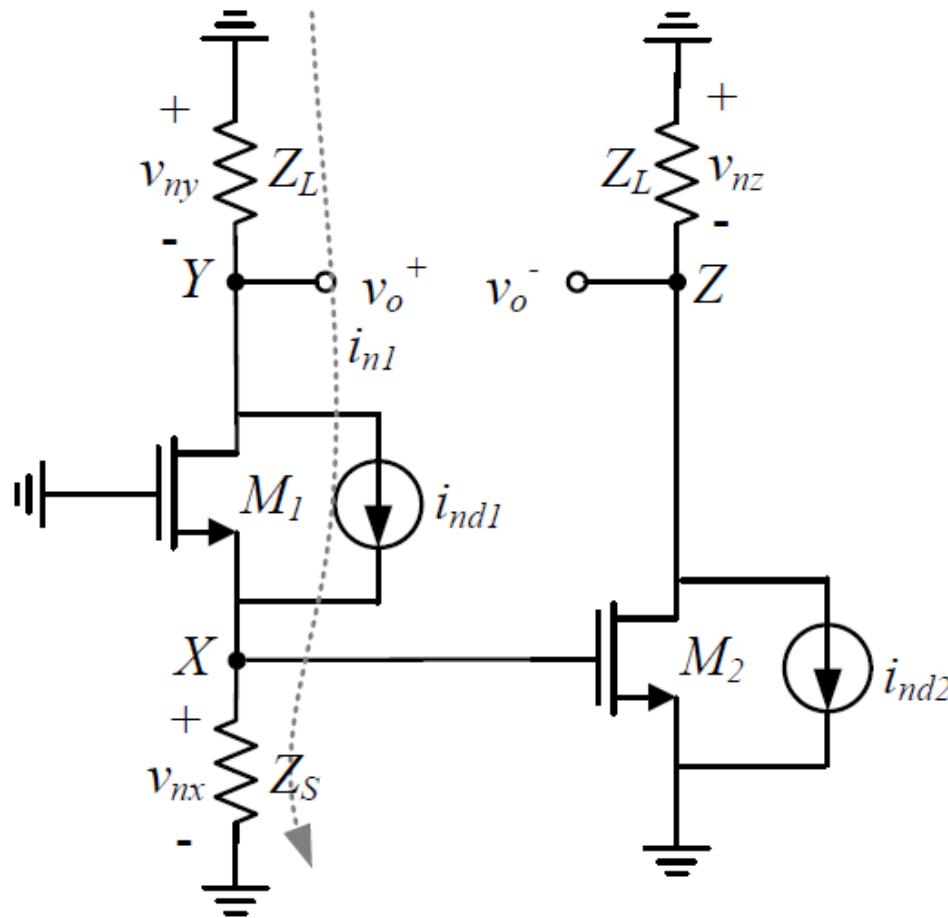


Output noise voltages:

$$\begin{aligned} v_o^+ - v_o^- &= v_{ny} - v_{nz} \\ &= i_{n1}(1 - g_{m2}Z_s)Z_L \end{aligned}$$

For cancellation:

$$g_{m2} = 1/Z_s = g_{m1}$$

The LNTA noise circuit model

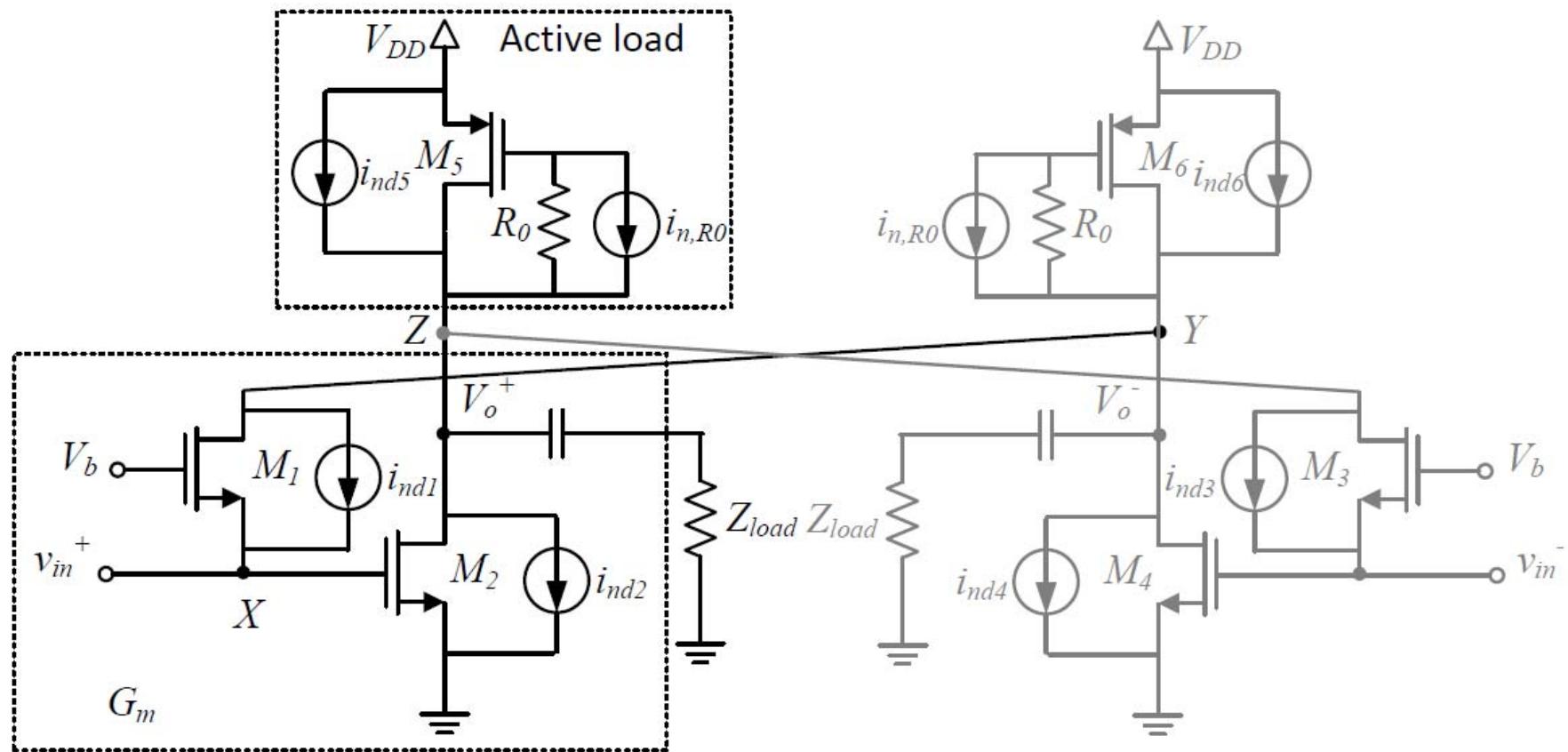



Noise Factor (thermal noise only)

Definition:

$$F = \frac{SNR_{in}}{SNR_{out}} = 1 + \frac{\overline{|i_{n,added}|^2}}{G_{m,eff}^2 \overline{|v_{ns}|^2}}$$

the added noise current is:

$$\overline{|i_{n,added}|^2} = \overline{|i_{n,G_m}|^2} + \overline{|i_{n,actLoad}|^2}$$

$$\overline{|i_{n,G_m}|^2} = \overline{|i_{n1}|^2}(g_{m2}Z_s - 1)^2 + \overline{|i_{nd2}|^2}$$

$$= \overline{|i_{n1}|^2}(g_{m2}Z_s - 1)^2 + 4kT\gamma_n g_{m2}$$

$$\overline{|i_{n,actLoad}|^2} = \overline{|i_{nd5}|^2} + \overline{|i_{n,R_0}|^2} = 4kT\gamma_p g_{m5} + \frac{4kT}{R_0}$$



Noise Factor

the source noise voltage is:

$$v_{ns} = \sqrt{4kTR_s} \frac{Z_{in,eff}}{R_s + Z_{in,eff}}$$

where,

$$Z_{in,eff} \approx \frac{r_{o1} + Z_L}{1 + (g_{m1} + g_{mb1})r_{o1}}$$

$$G_{m,eff} \approx \frac{1 + (g_{m1} + g_{mb1})r_{o1}}{r_{o1} + Z_L} + \frac{g_{m2}r_{o2}}{r_{o2} + Z_L}$$

and substituting...

$$F = 1 + \frac{\overline{|i_{n1}|^2}(g_{m2}R_s - 1)^2}{4kTR_s^{-1}(R_s \parallel Z_{in,eff})^2 G_{m,eff}^2} + \frac{r_n g_{m2} + r_p g_{m5} + R_0^{-1}}{R_s^{-1}(R_s \parallel Z_{in,eff})^2 G_{m,eff}^2}$$

$$F = 1 + 4 \frac{r_n g_{m2} + r_p g_{m5} + R_0^{-1}}{R_s G_{m,eff}^2} = 1 + 4 \frac{r_n g_{m2} + r_p g_{m5} + R_0^{-1}}{\left[\frac{1 + (g_{m1} + g_{mb1})r_{o1}}{Z_L + r_{o1}} + \frac{g_{m2}r_{o2}}{Z_L + r_{o2}} \right]^2 R_s}$$

Conclusion



- Fully differential OTAs offer the greatest versatility and system design possibilities.
- OTAs can be used to implement more complex microwave circuits while keeping chip dimensions small.
- Reducing the NF of OTAs continues to be an active area of investigation.

References



1. R. L. Geiger and E. Sanchez-Sinencio, "Active filter design using operational transconductance amplifiers: a tutorial," *IEEE Circuits and Devices Magazine*, vol.1, no.2, pp.20,32, March 1985.
2. J. Xu, C. E. Saavedra and G. Chen, "5.4 GHz reconfigurable quadrature amplitude modulator using very high-speed OTAs," *IEEE International Microwave Symposium*, pp.1-4, June 2011.
3. You Zheng and C. E. Saavedra, "Active Quasi-Circulator MMIC Using OTAs," *IEEE Microwave and Wireless Components Lett.*, vol.19, no.4, pp.218-220, April 2009.
4. Jiangtao Xu, C. E. Saavedra and Guican Chen, "A 12 GHz-Bandwidth CMOS Mixer With Variable Conversion Gain Capability," *IEEE Microwave and Wireless Components Lett.*, vol.21, no.10, pp.565-567, Oct. 2011.
5. You Zheng and C. E. Saavedra, "Feedforward-Regulated Cascode OTA for Gigahertz Applications," *IEEE Trans. Circuits and Systems I: Regular Papers*, vol.55, no.11, pp.3373-3382, Dec. 2008.
6. You Zheng and C. E. Saavedra, "An Ultra-Compact CMOS Variable Phase Shifter for 2.4-GHz ISM Applications," *IEEE Trans. Microwave Theory and Techniques*, vol.56, no.6, pp.1349-1354, June 2008.
7. You Zheng and C. E. Saavedra, "Full 360 Vector-Sum Phase-Shifter for Microwave System Applications," *IEEE Trans. Circuits and Systems I: Regular Papers*, vol.57, no.4, pp.752,758, April 2010.
8. Jiangtao Xu, C. E. Saavedra and Guican Chen, "Wideband microwave OTA with tunable transconductance using feedforward regulation and an active inductor load," *IEEE NEWCAS Conf.* pp.93-96, June 2010.
9. F. Brucolieri, E.A.M. Klumperink, B. Nauta, "Wide-band CMOS low-noise amplifier exploiting thermal noise canceling," *IEEE J. Solid-State Circuits*, vol.39, no.2, pp.275,282, Feb. 2004.
10. F. Jiang, "Broadband low-noise CMOS mixers for wireless communications", *Master of Applied Science Thesis*, Queen's University, Kingston, Ontario, Canada, 2013.
11. Jiangtao Xu, C. E. Saavedra and Guican Chen, "Noise analysis of the CG-CS low noise transconductance amplifier," *IEEE Int. Conf. Electron Devices and Solid-State Circuits (EDSSC)*, pp.1-2, Nov. 2011.